

# ***A NEW FEED SYSTEM FOR ARRAYS***



By John Devoldere, ON4UN  
Robye Lahlum, W1MK  
Roger Vermet, ON6WU

© ON4UN

## ***NEW FEED SYSTEM FOR ARRAYS***



- Arrays on Low Bands often have all elements fed
- Not necessarily: see N7JW
- What is the best feed method?
  - Easiest, “plug and play”
  - Most flexible (optimized results)
  - How much better ?

© ON4UN

## PHASING ANGLE & LINE LENGTH

- In the past:  
phase delay =  
cable length
- IS WRONG  
(in most cases)

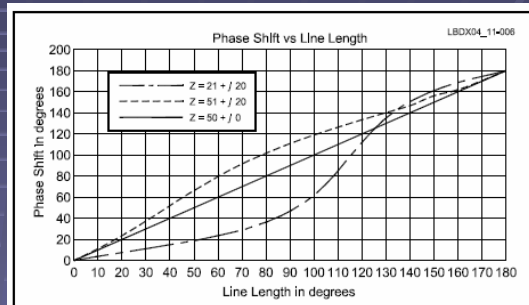


Fig 11-6—Graph showing the current phase shift in a 50- $\Omega$  line (RG -213, on 80 meters), as a function of the load impedance. The loads shown are those for a 2-element cardioid array. Note that the phase shift does *not* equal line length, except when the line is terminated in its own characteristic impedance!

© ON4UN


## BREAKTHROUGHS

- Forest Gehrke – K2BT- Ham Radio 1983
- W2CQH: the hybrid coupler QST Jan 1978

© ON4UN
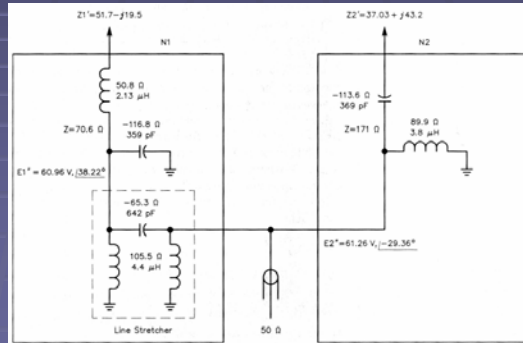
# GEHRKE – K2BT METHOD


Gehrke, K2BT, has developed a technique that is fairly standard in the broadcast world.




Typical K2BT feed system for a 2-element array

© ON4UN

# THE HYBRID COUPLER

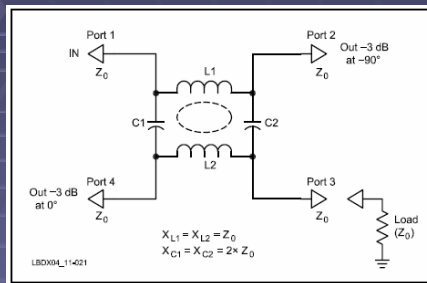

(Commercialized by COMTEK)

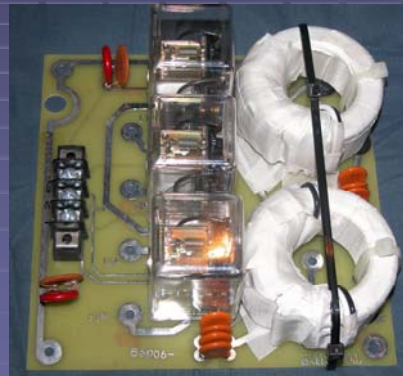

© ON4UN

## OTHER SYSTEMS

- Many other systems e.g. K3LC, W8JI (cross fire) etc.

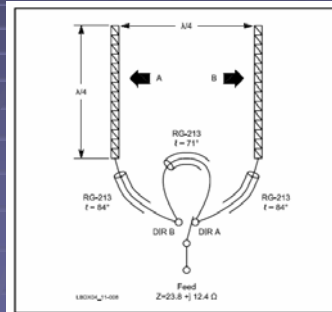


Fig 11-8—Christman feed system for the 2-element  $\lambda/4$ -spaced cardioid array fed  $90^\circ$  out-of-phase. Note that the two feed lines are  $94^\circ$  long (not  $90^\circ$ ), and that the “ $90^\circ$  phasing line” is actually  $71^\circ$  electrical degrees in length. The impedance at the connection point of the two lines is  $23.8 + j12.4 \Omega$  (representing an SWR of 2.3:1 for a  $50\text{-}\Omega$  line), so some form of matching network is desirable.

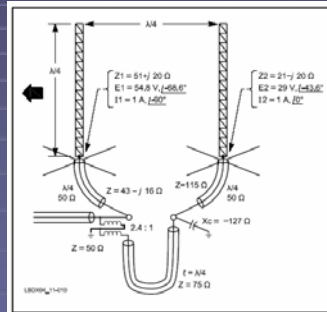


Fig 11-10—While all other feed methods feed the back element directly and provide phase delay via coaxial cable or a network to the front element, the cross-fire feeding system does the opposite. It makes use of a  $180^\circ$  phase-inverter transformer to achieve a feed system that guarantees that the phase delay remain correct when the frequency is changed. See text for details.

© ON4UN

## W7EL's BREAKTHROUGH

- W7EL current forcing
  - Covered in great detail in ARRL Antenna book
  - Property of a quarter wave long feed line:

$$I(\text{at ant}) = E(\text{at end line}) / Z_{\text{cable}}$$

- $I(\text{at antenna})$  determines radiation (not  $E!$ )
- $E$  is easier to measure than  $I$
- So: measure  $E$  at the end of a  $\frac{1}{4}$  wave line

© ON4UN

## ***NOW: FULL DESIGN FREEDOM***

### **W7EL L network → W1MK L network**

- Until now formulas available only for quadrature feed but with any feed current magnitude  
( Quadrature = in increments of 90 deg )
- **Now W1MK developed the mathematics that apply for any magnitude and phase angle**
- It really is a Gehrke equivalent (= FULL DESIGN FREEDOM) where all networks are combined in a single L network


© ON4UN

## ***WHY?***

- Why do we want “any” magnitude and phase angle?
  - More design freedom for improved performance
  - Let’s analyze the well known 4-square array


© ON4UN

# OPTIMIZED VS. QUADRATURE

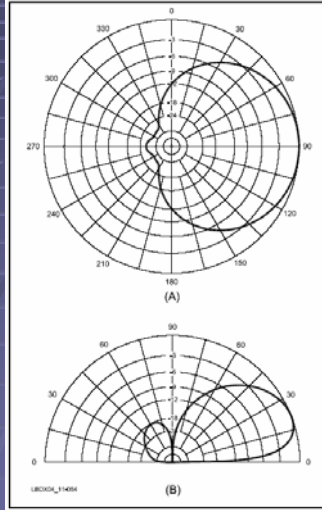
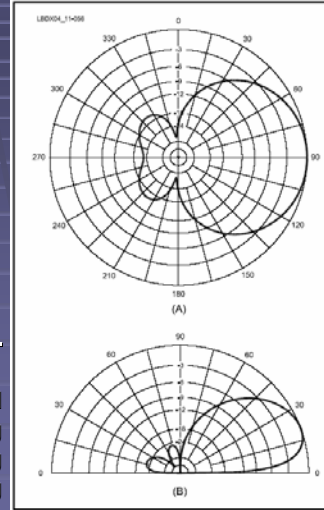
## LEFT:

Quadrature feed with equal currents  
 Back: 1A at 0 deg  
 Cntr: 1A at -90 deg  
 Frnt: 1A at -180 deg



## RIGHT:

WA3FET feed  
 Back: 1A at 0 deg  
 Cntr: 0.9A at -111 deg  
 Frnt: 0.872A at -218deg

G = 6.7 dBi, RDF = 10.6 dB, DMF = 21.0 dB


G = 7.2 dBi, RDF = 11.4 dB, DMF 24.0 dB

© ON4UN

# QUADRATURE
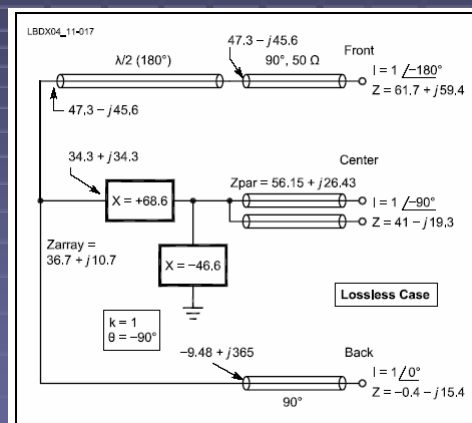
## Quadrature feed

Can be calculated with W7EL formulas from ARRL Antenna Book



Or you can use a hybrid coupler!

© ON4UN

# FULL FREEDOM


## Odd phase angles (non quadrature)

- No calculation tool so far
- **Now the mathematics and a user tool are introduced by W1MK**

© ON4UN
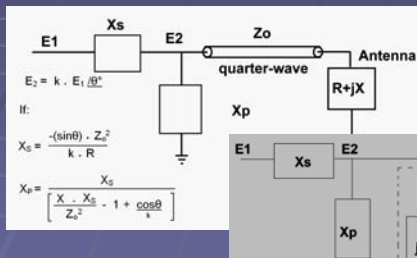
# WA3FET OPTIMIZED FEED

- Networks to be calculated with W1MK's formulas





$$E_2 = k \cdot E_1 / \theta$$

if:

$$X_s = \frac{-\sin(\theta) \cdot Z_o^2}{k \cdot R}$$
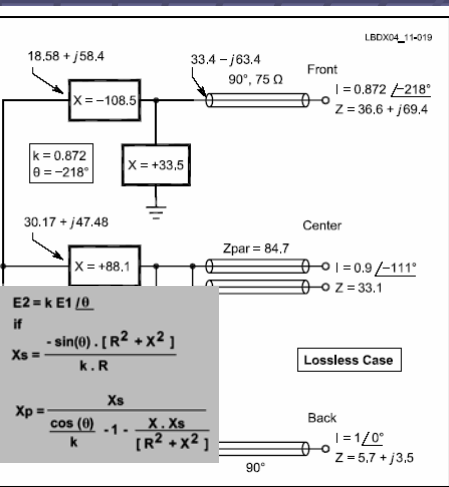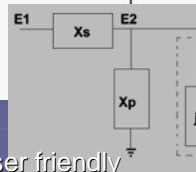
$$X_p = \frac{X_s}{\left[ \frac{X_s - X_o}{Z_o^2} - 1 + \frac{\cos \theta}{k} \right]}$$




- Used in a user friendly Excel spreadsheet

© ON4UN

W1MK

## EQUATIONS FOR ANY AMP/PHASE

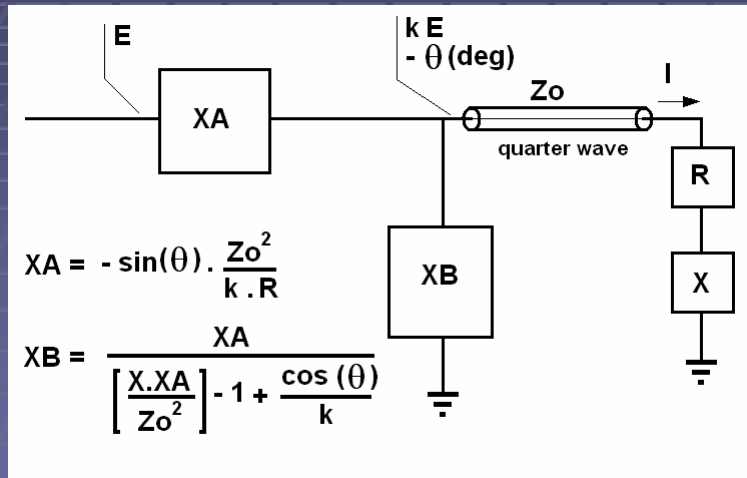

W1MK

## COMPARISON

### W7EL

$$k = 1$$

$$\theta = -90 \text{ deg}$$

$$X_A = \frac{Z_o^2}{R}$$

$$X_B = \frac{X_A}{\left[ \frac{X \cdot X_A}{Z_o^2} \right] - 1}$$

### General Solution (W1MK)

$$k = \text{variable (amplitude)}$$

$$\theta = \text{variable (phase, degrees)}$$

$$X_A = -\sin(\theta) \cdot \frac{Z_o^2}{k \cdot R}$$

$$X_B = \frac{X_A}{\left[ \frac{X \cdot X_A}{Z_o^2} \right] - 1 + \frac{\cos(\theta)}{k}}$$

W1MK




# THE SPREADSHEET TOOL (1)

## CALCULATION L-NETWORK FOR LEWALLEN / LAHLUM F

For system using current forcing

INPUT DATA		
n elem	1	
Zo	75.00	ohm
R	36.60	ohm
X	69.40	ohm
k	0.87	
theta	-218.00	deg
freq	1.83	MHz
RESULTS		
X-Series	-108.51	ohm
X-Par	33.46	ohm
Series elem	801.9	pF
Par elem	2.9	uH
Rpar	202.12	ohm
Xpar	-64.31	ohm
Rser	18.58	ohm
Xser	-58.40	ohm

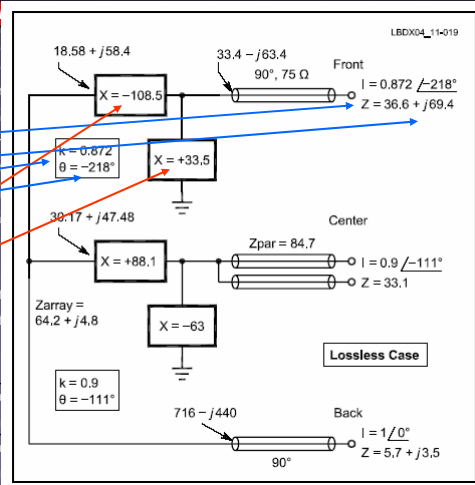


© ON4UN

# THE SPREADSHEET TOOL (2)

## CALCULATION L-NETWORK FOR LEWALLEN / LAHLUM F

For system using current forcing


INPUT DATA		
n elem	2	
Zo	75.00	ohm
R	33.10	ohm
X	0.00	ohm
k	0.90	
theta	-111.00	deg
freq	1.83	MHz
RESULTS		
X-Series	88.14	ohm
X-Par	-63.04	ohm
Series elem	7.7	uH
Par elem	1390.3	pF
Rpar	104.90	ohm
Xpar	66.65	ohm
Rser	30.17	ohm
Xser	47.48	ohm

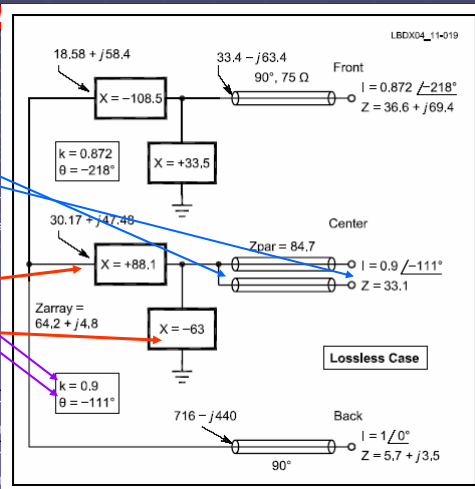

© ON4UN
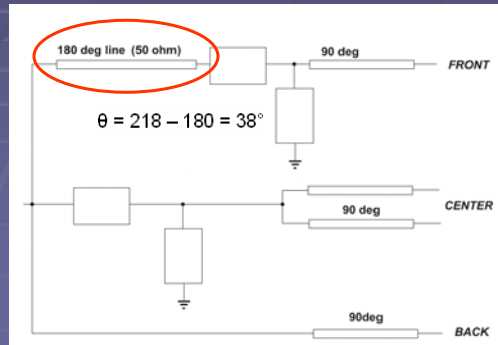
## THE 180 DEGREE LINE

You can also feed the front element through a 180 (half wave) line, in which case The L network will add  $218 - 180 = 38$  deg of phase shift



© ON4UN

INPUT DATA		
n elem	1	
Zo	75.00	ohm
R	36.60	ohm
X	69.40	ohm
k	0.87	
theta	-38.00	deg
freq	1.83	MHz
RESULTS		
X-Series	108.51	ohm
X-Par	87.34	ohm
Series elem	9.4	uH
Par elem	7.6	uH
Rpar	202.12	ohm
Xpar	346.84	ohm
Rser	150.88	ohm
Xser	87.93	ohm

## GETTING PRACTICAL

After the PAPERWORK, let's DO it.

- Our goal:
  - Rebuild the ON4UN 4-square (80m)
  - Install a hybrid coupler system
  - Develop, build and test a Lewallen/Lahlum system
  - Measure current and phase on both systems
  - Assess and evaluate results of both systems


Thank you Jay, WX0B, for helping with the one of your 4-square boxes boxes



© ON4UN
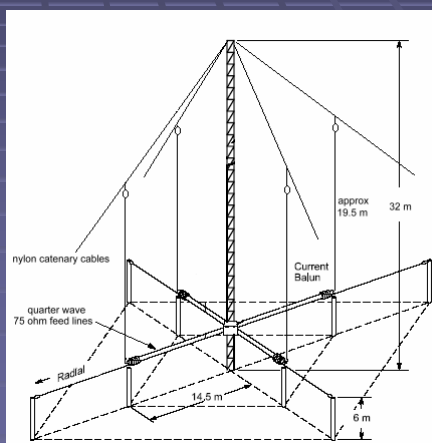
## EXPERIMENTS AT ON4UN

- Rebuild the 4-square
  - New elements
  - New feed points
  - New quarter-wave feed lines
  - Switchable to 3.505 or 3.795 MHz



© ON4UN

## THE ON4UN 80M 4-SQUARE



by ON4UN



ELEVATED FEED POINT 4-SQUARE ELEMENT

by ON4UN

© ON4UN

## THE ON4UN 80M 4-SQUARE




© ON4UN

## DESIGNING THE NETWORK

- **Calculating the Lahlum-Lewallen network**
  - Model the array (Eztec)
  - Build the array
  - Resonate the elements
  - Measure the  $Z = R$  at resonance for each element (should be close)
  - Model a single element
  - Add  $R_{loss}$  (as a series  $R$  at the feed point) to obtain same feed impedance as measured
  - Remodel the array with these loss resistors
  - Plug in the  $Z$  obtained  $Z$ -values in the Lahlum spreadsheet tool

© ON4UN

# THE MODEL

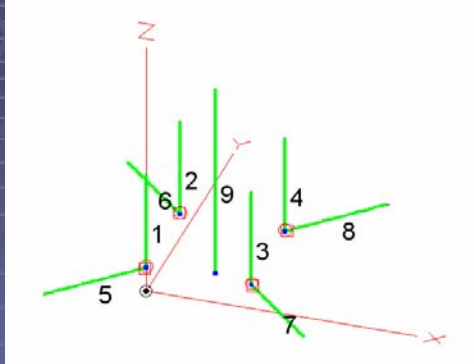


- Source 1 Voltage = 20.78 V. at 29.08 deg.  
Current = 1.66 A. at 0.0 deg.  
Impedance =  $18.16 + j 10.1$  ohms  
Power = 18.10 watts  
SWR (50 ohm system) = 2.881 (75 ohm system) = 1.715
- Source 2 Voltage = 32.36 V. at -111.71 deg.  
Current = 1.11 A. at -111.0 deg.  
Impedance =  $29.15 - j 0.3587$  ohms  
Power = 35.92 watts  
SWR (50 ohm system) = 1.715 (75 ohm system) = 1.715
- Source 3 Voltage = 32.36 V. at -111.71 deg.  
Current = 1.11 A. at -111.0 deg.  
Impedance =  $29.15 - j 0.3614$  ohms  
Power = 35.92 watts  
SWR (50 ohm system) = 1.715 (75 ohm system) = 1.715
- Source 4 Voltage = 103.6 V. at -174.94 deg.  
Current = 1.666 A. at 218.0 deg.  
Impedance =  $45.44 + j 42.46$  ohms  
Power = 126.1 watts  
SWR (50 ohm system) = 2.383 (75 ohm system) = 1.715

Sources						
No.	Specified Pos.	Actual Pos.	Amplitude	Phase	Ty	
Wire #	% From E1	% From E1	Seg	[V, A]	[deg]	
1	1	1.66667	1	1	0	I
2	2	1.66667	1	1.11	-111	I
3	3	1.66667	1	1.11	-111	I
4	4	1.66667	1	1.666	-218	I

Loads (R + jX)						
No.	Specified Pos.	Actual Pos.	R	X		
Wire #	% From E1	% From E1	Seg	[ohms]	[ohms]	
1	5	1.66667	1	10	0	
2	6	1.66667	1	10	0	
3	7	1.66667	1	10	0	
4	8	1.66667	1	10	0	

© ON4UN

# FEED SYSTEM AFTER MODEL

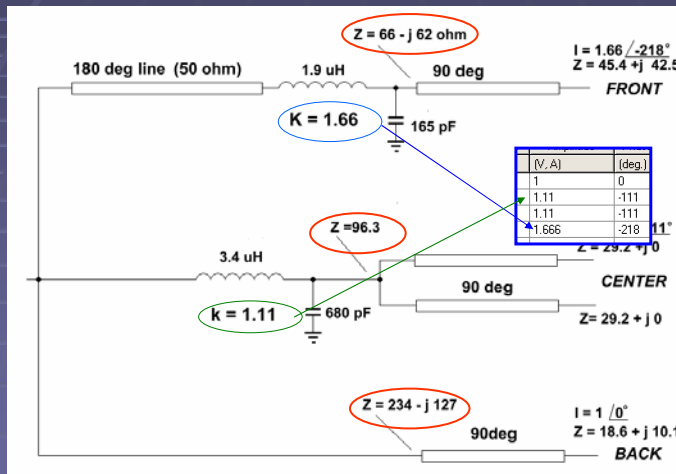

© ON4UN

# WORK IN THE WORKSHOP

## WHY?



- Verify the feasibility of the L-networks approach
- Develop an appropriate test and measurement method, to adjust the values of the L networks
- Evaluate the test method

In a first iteration this was done on dummy loads  
(also to stay out of the rain...)

© ON4UN
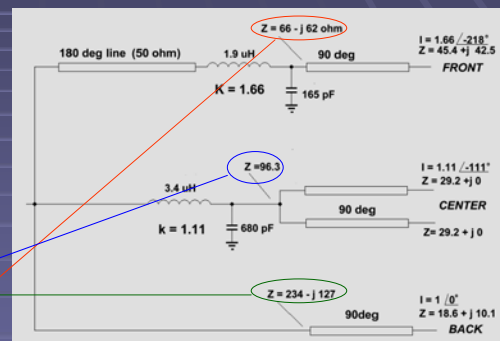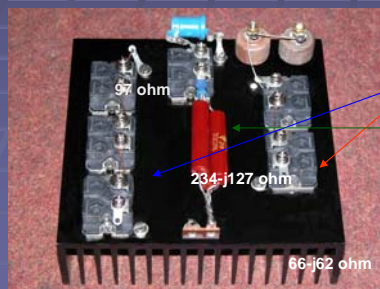
# THE DUMMY LOADS

Build dummy loads representing the complex impedances at the end of the quarter-wave feed lines





The loads are capable of dissipating hundreds of Watts.

© ON4UN
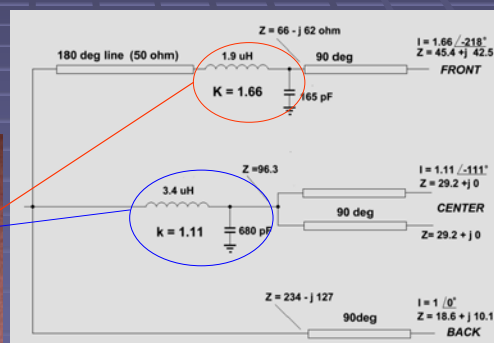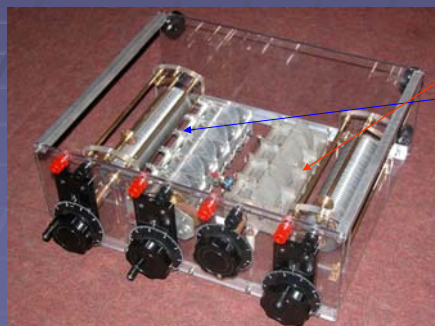
## THE LC NETWORKS

Build an LC box with two variable L's and two variable C's



© ON4UN

## THE ALIGNMENT TOOL

### THE SCOPE PROCEDURE

- Use a multi channel oscilloscope
- Simultaneously visualize the voltages at the end of the quarter-wave feed lines
- Voltage = antenna feed current x  $Z_{\text{cable}}$  plus 90 degree phase delay


© ON4UN

# THE MULTI CHANNEL SCOPE

We used a 5 channel 100 MHz scope (Kikusui - model COS6100M )

Available on Ebay for approx. \$200


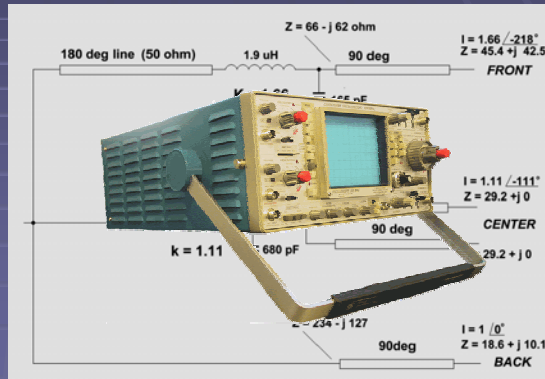
A 3 channel scope is really all you need ...



© ON4UN

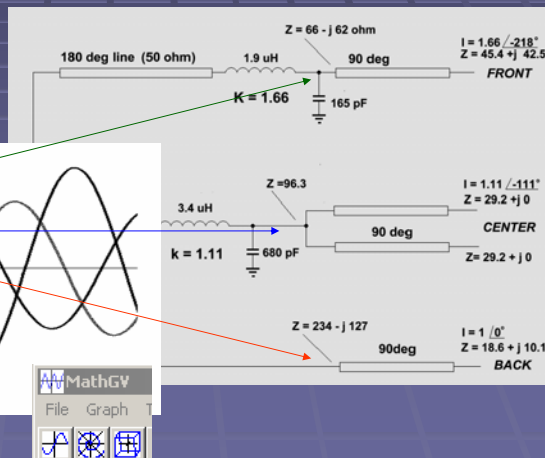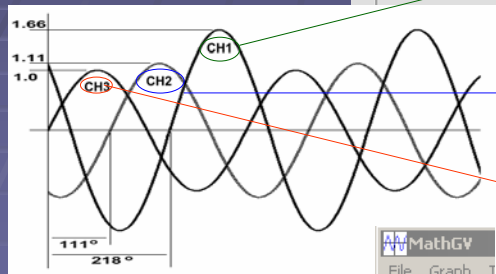
# THE SCOPE PATTERN

- CH3 is the reference signal (back element)
- CH2 is the signal going to the center elements
- CH1 is the signal going to the front element



© ON4UN



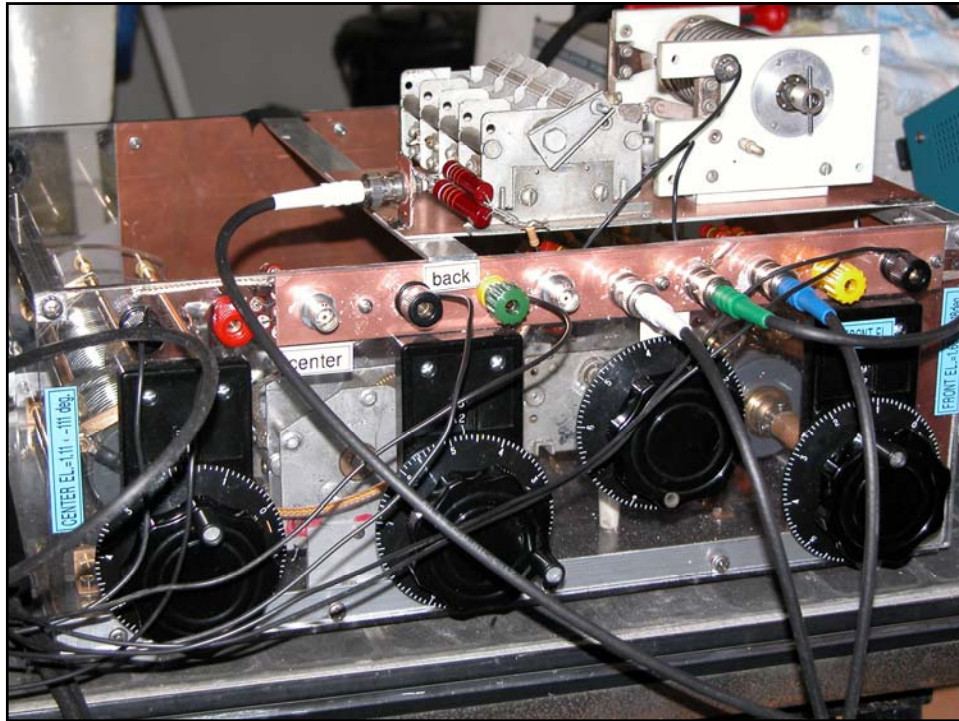

## THE VOLTAGE SAMPLING

Samplers:


$Z_{load} = 12.5 \text{ k}$ , attenuation is  $12500/25 = 500 = -54 \text{ dB}$

Channel 3: the reference signal going to the back element (no network)

Channel 2: the measured signal at the output of LC network going to the center elements


Channel 1: the measured signal at the output of LC network going to the front element

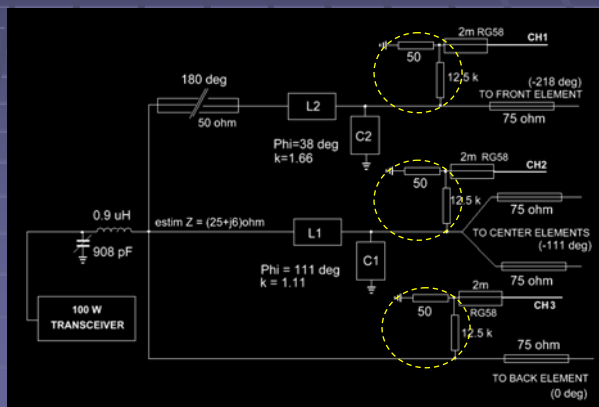The LC components are tuned until the required phase shift and voltage are achieved.



# THE SCOPE PATTERN

Just a drawing ...

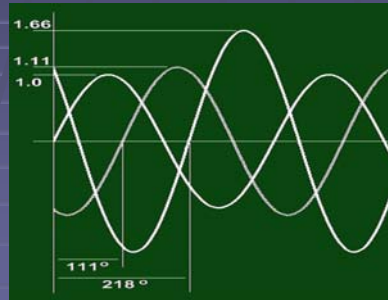


MADE WITH




© ON4UN

# THE SCOPE PATTERN

On the multi-channel scope

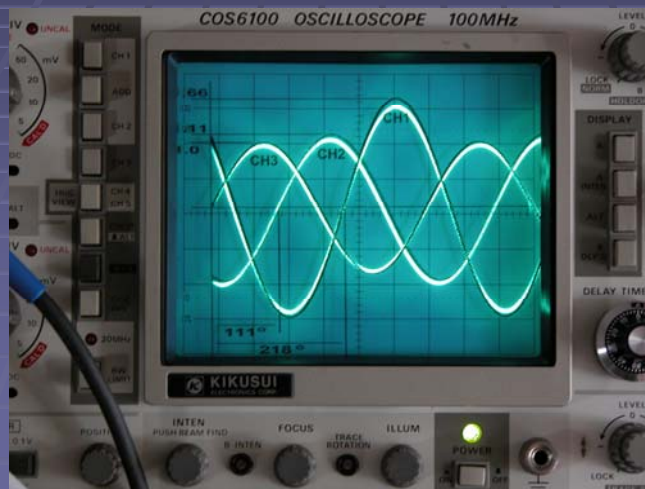

© ON4UN

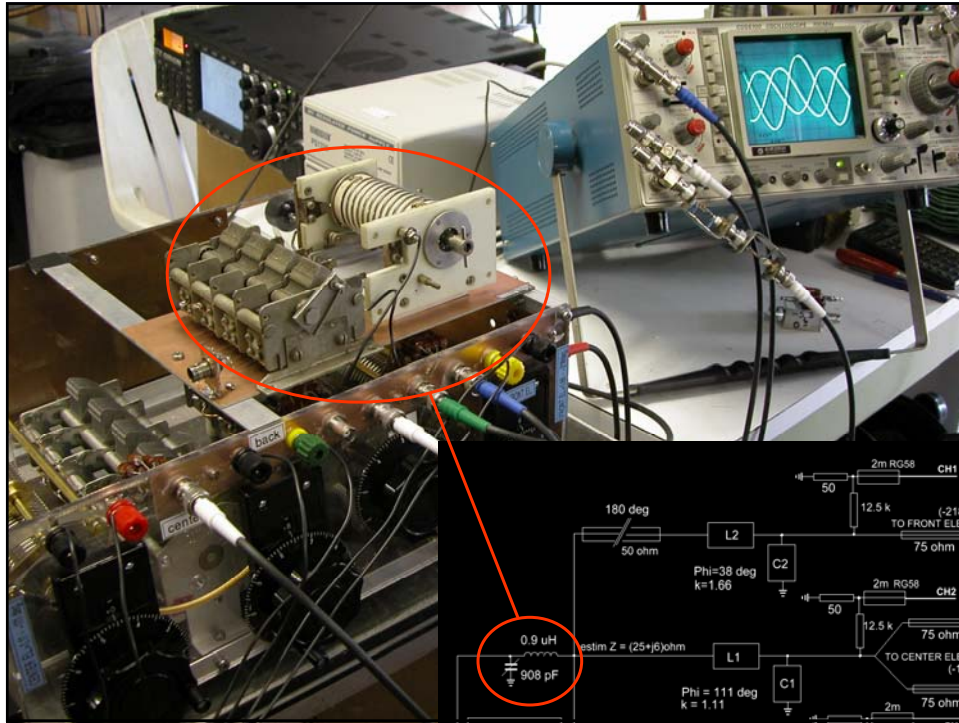

## SCOPE PROCEDURE

- Dummies:  $230 - j 120$ ,  $97$  and  $66 - j 62$  ohm
- L1, C1: to center elements, L2, C2 to front element

	model	dummy
L1 (ser)	3.4 uH	3.4 uH
C1 (par)	680 pF	818 pF
L2 (ser)	1.9 uH	1.4 uH
C2 (par)	165 pF	530 pF

- Feed impedance:  $19.7 + j 8$  ohm

© ON4UN

## A CONCLUSION


- ALIGNMENT PROCEDURE WAS VALIDATED
- ALIGNMENT EASY BUT CRITICAL (TOUCHY)


**NEXT STEP:**

**WAIT FOR BETTER WX AND GO OUT IN THE FIELD**

© ON4UN



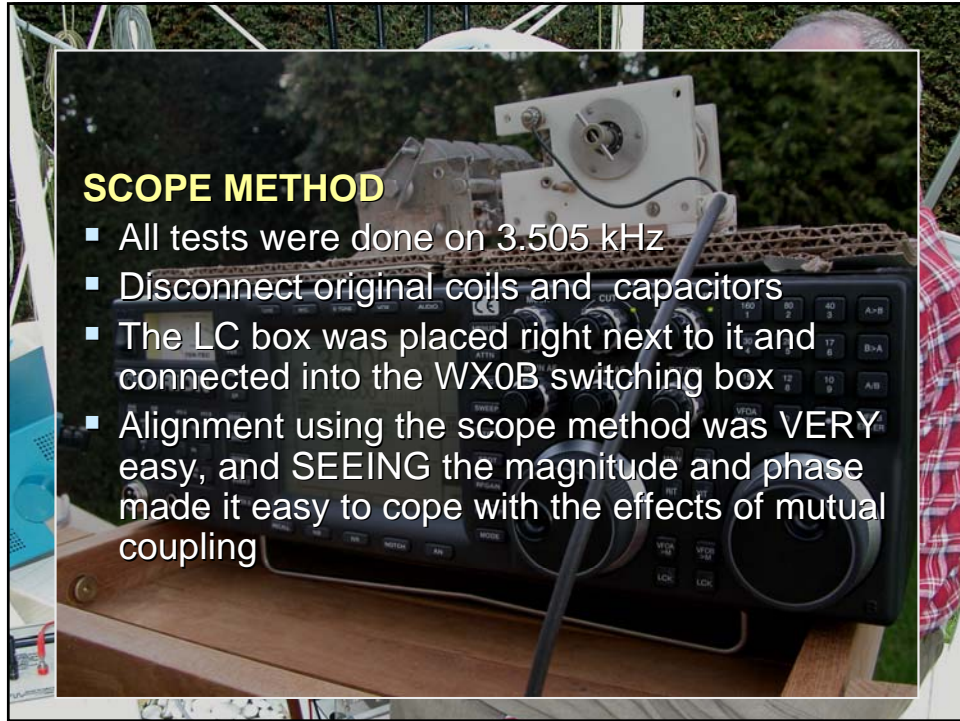

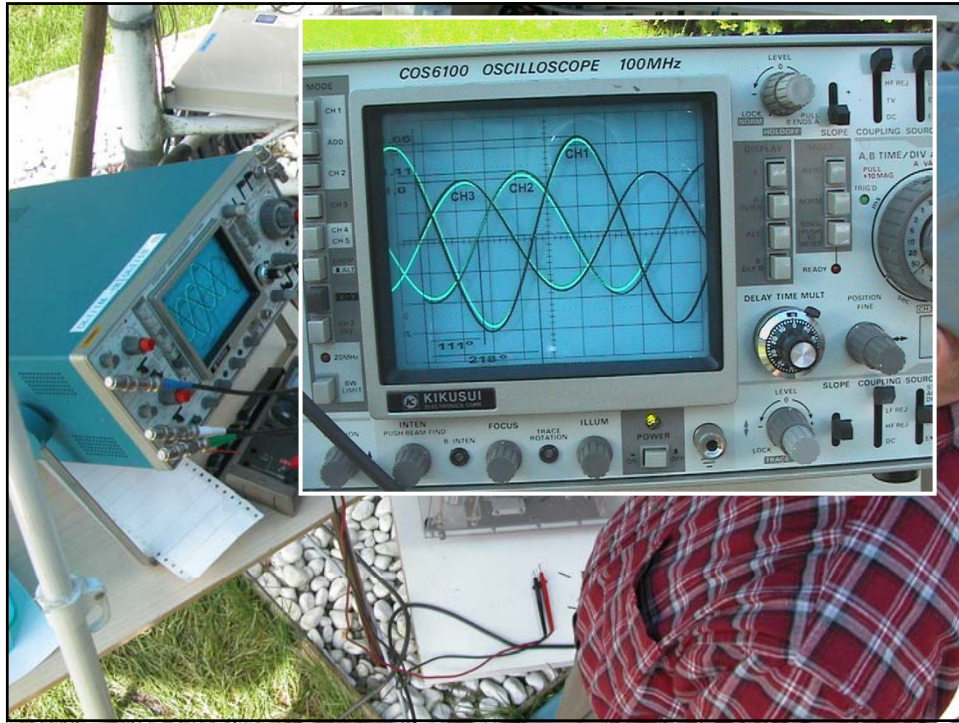

## LC NETWORK DIAL SETTINGS

	C1	L1	C2	L2
NW	31.66	25.63	17	32.83
SE	30.94	25.31	19	35.16
NE	29.90	26.11	17	34.69
SW	31.29	25.28	16	33.13

FINAL	30.83	25.66	17.5	34.22
VALUES	3.3 uH	283 pF	867 pF	1.6 uH

# VARIATIONS IN AMP AND PHASE


TARGET	1.11	-111°	1.66	-218°
--------	------	-------	------	-------

	K1	$\varphi 1$	K2	$\varphi 2$
NW	1.01	-115°	1.52	-210°
SE	1.15	-111°	1.68	-222°
NE	1.19	-111°	1.66	-222°
SW	1.08	-118°	1.69	-218°

Accuracy: phase +/- a few degrees, amplitude +/- 2 %

# IN REALITY
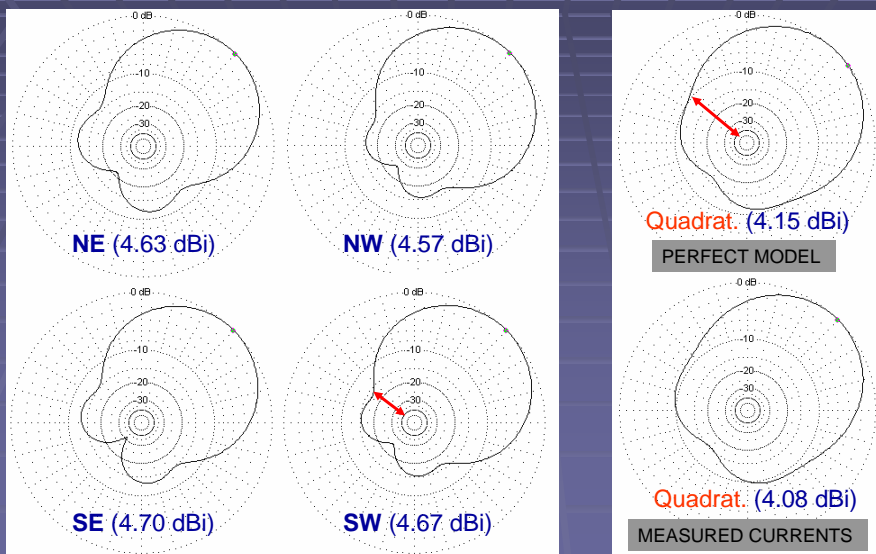
## INFLUENCE OF LESS THAN PERFECT RESULTS



# IN REALITY

## INFLUENCE OF LESS THAN PERFECT RESULTS

### SUMMARY:

Quadrature (hybrid): <1dB less Gain

- 0.6 dB forward gain
- 0.1 dB (max) dummy power

Side reject. approx 8dB (vs. 15 dB)

On RX: inferior

On TX: ~ 0.7 dB TOTAL (17% in POWER)

SE (4.70 dBi)

SW (4.67 dBi)

MEASURED CURRENTS

## MORE TESTS WERE DONE

- TO ASSESS OPERATIONAL BANDWIDTH
- ... AND SWR BANDWIDTH






## OPERATIONAL BANDWIDTH

	K1	$\phi 1$	K2	$\phi 2$
3.500	1.15	-102°	1.6	-210°
3.520.000	1.11	-111°	1.66	-218°
3.540	1.05	-120°	1.70	-230°


- OPERATIONAL BW: ~ 50 kHz
- SWR = 1/1 OVER APPROX. 100 kHz
- SWR BW IS NO VALID PERFORMANCE CRITERION

## OPERATIONAL BANDWIDTH


### PATTERNS VS. FREQUENCY

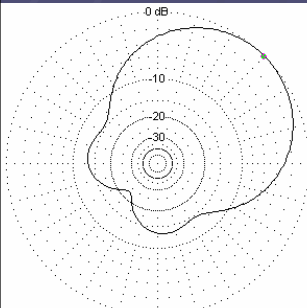

3500 KHz (4.64 dBi)

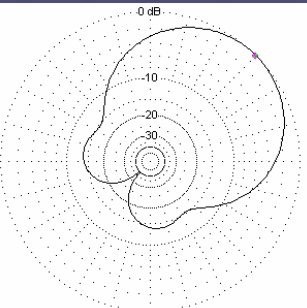

3520 kHz (4.62 dBi)

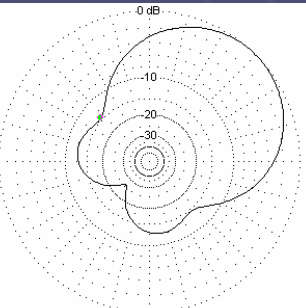

3540 KHz (4.61 dBi)

## **CONCLUSION ON SCOPE PROCEDURE**

- HIGH DRIVING POWER REQUIRED (100 W) BECAUSE OF “LOW” SCOPE SENSITIVITY
- EXCELLENT HUMAN INTERFACE (YOU SEE WHAT YOU DO)
- SUFFICIENT ACCURACY IN VIEW OF DIFFERENCES BETWEEN DIRECTIONS (SLIGHT DIFFERENCES IN ELEMENT SELF AND MUTUAL IMPEDANCES)

© ON4UN

## **MORE CONCLUSIONS**

- L NETWORK COMPONENTS MUST BE CONTINUOUSLY ADJUSTABLE
- ARRAY ELEMENTS ARE NOT “IDENTICAL”
- ACCURACY OF ALIGNMENT METHOD SHOULD NOT BE “MUCH” BETTER THAN VARIATION IN ELEMENT IMPEDANCES (don’t measure a mile with a micrometer)

# BUILDING A NEW HIGH POWER SYSTEM

- CONTINUOUSLY VARIABLE CAPS: VACUUM VARIABLES
- CONTINUOUSLY VARIABLE CAPS: VERY BULKY FOR HIGH POWER
- THE SOLUTION: IS IN "THE BOOK" :

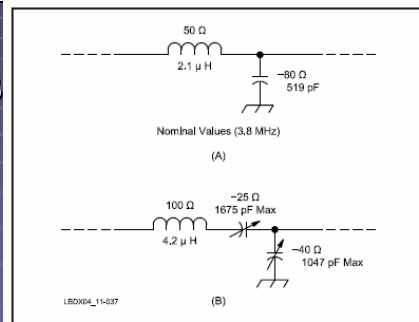


Fig 11-37—To make the Lewallen L-network continuously adjustable, replace the coil with a coil of twice the required value and connect a capacitor in series. The net result will be a continuously variable reactance. With the values shown, the nominal +50- $\Omega$  reactance is adjustable from +75 to +25  $\Omega$  (and less). The two capacitors can be motor driven to make the phase-shift network remotely controllable.

## TURNING A C INTO AN L


Center elements:

target L: 75 ohm or 3.4 uH

Top of tuning range = 4.6 uH  $\rightarrow$  100  $\Omega$

1200 pF = -38  $\Omega$

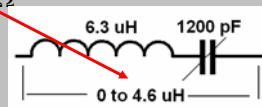Coil: 100 + 38 = 138 ohm  $\rightarrow$  6.3 uH




Front element

Target L: 35 ohm or 1.6 uH

Top of tuning range = 3 uH  $\rightarrow$  65  $\Omega$

1200 pF = -38  $\Omega$

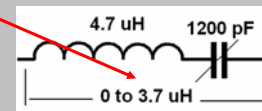Coil = 65 + 38 = 103  $\Omega$   $\rightarrow$  4.7 uH




# THE NEW FEED BOX



- USING FOUR 1200 pF VACUUM VARIABLES EQUIPED WITH TURN COUTERS
- VACUUM VARIABLE C IN SERIES WITH AN “OVERSIZED” COIL TO FORM A VARIABLE L
- RELAY MATRIX SWITCHING TO PROVIDE MAX. SYMMETRY AND FLEXIBILITY
- SEPARATE INPUT MATCHING L- NETWORKS FOR 4-SQUARE AND OMNIDIRECTIONAL


© ON4UN



# THE NEW BOX SCHEMATIC

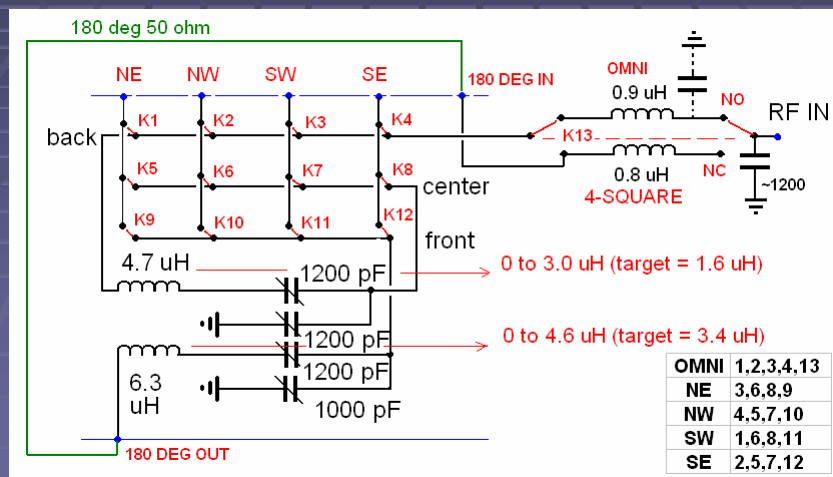


© ON4UN

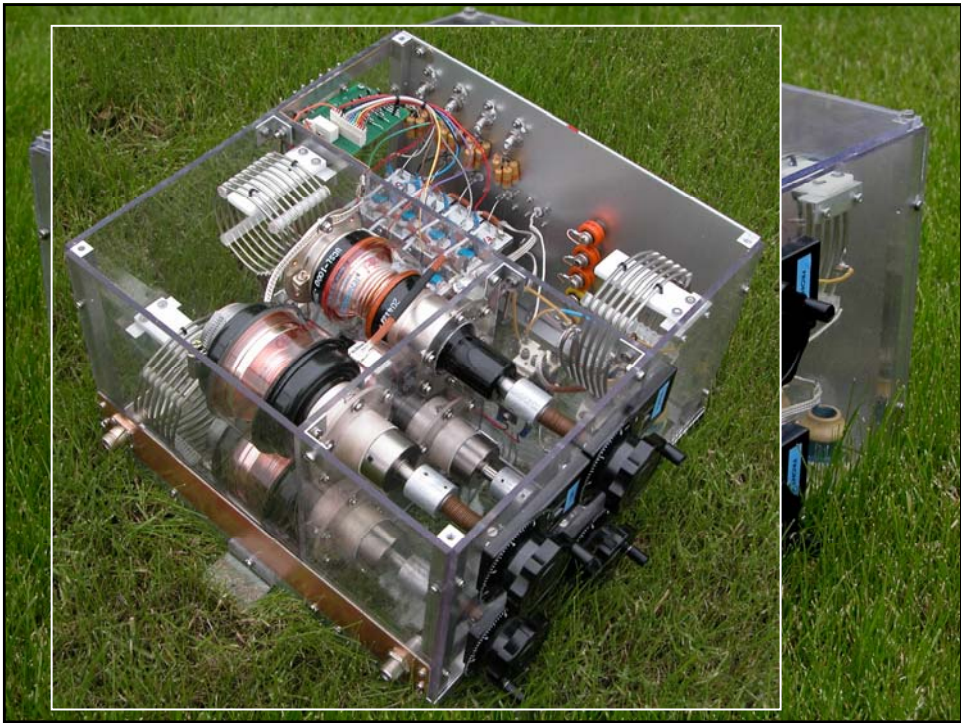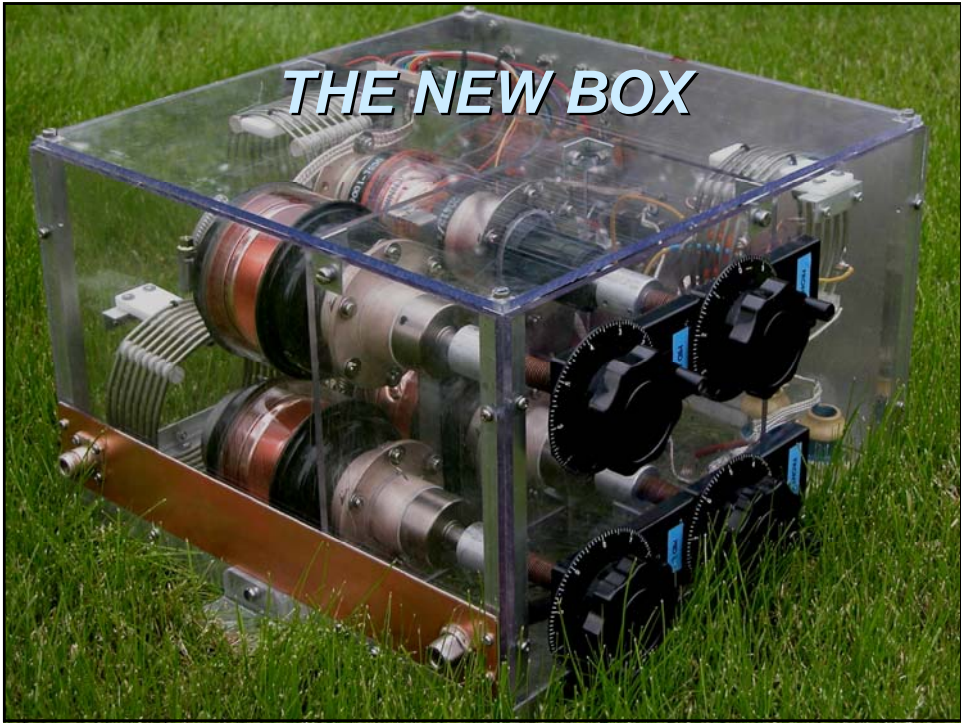


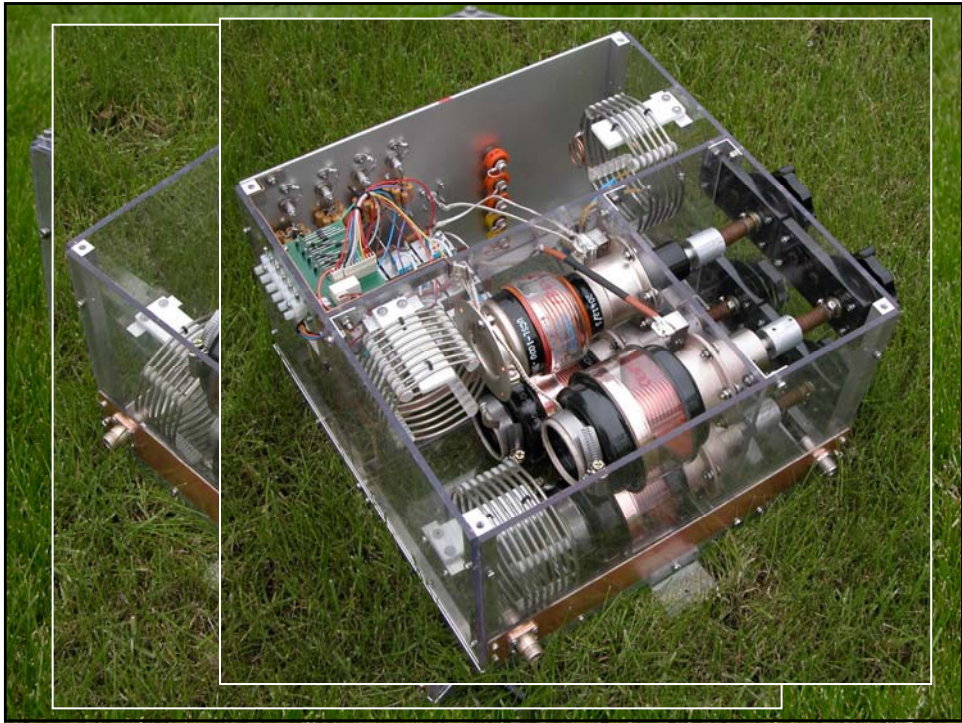


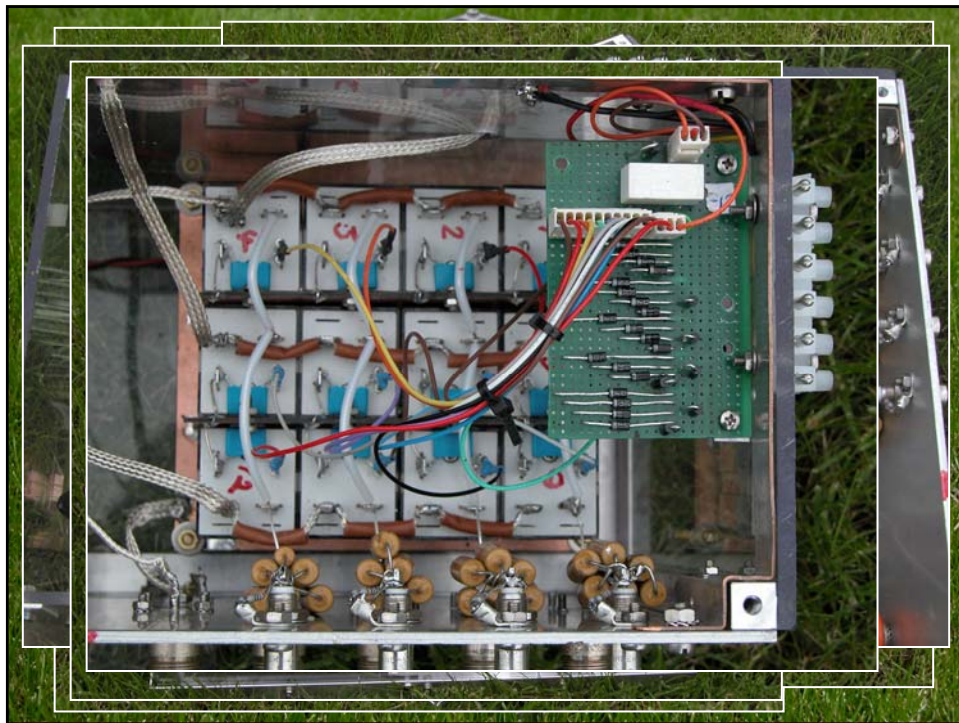
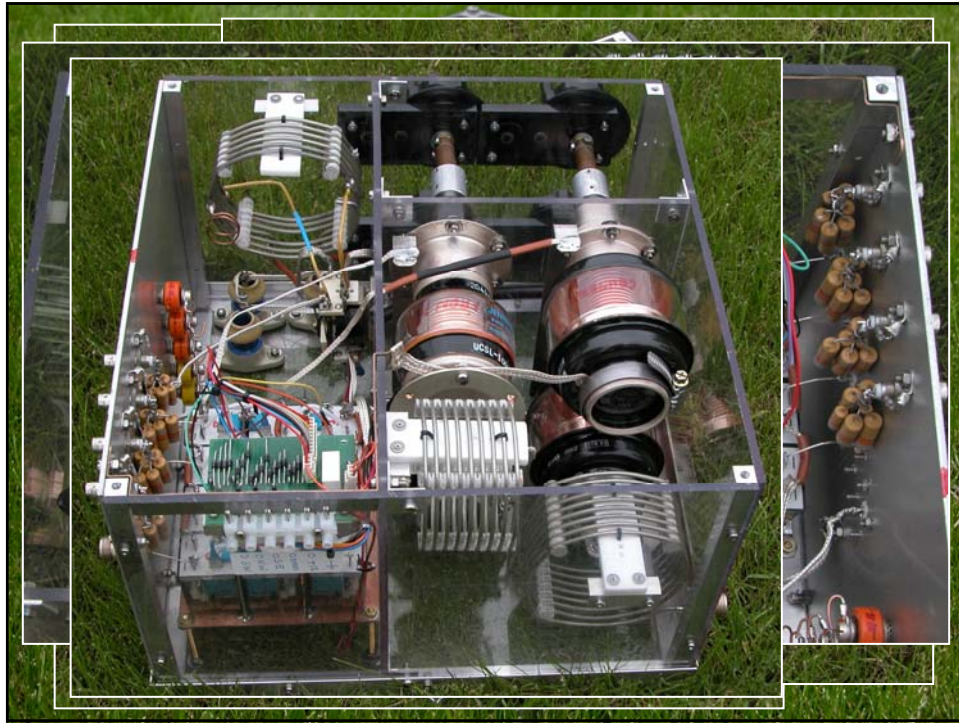


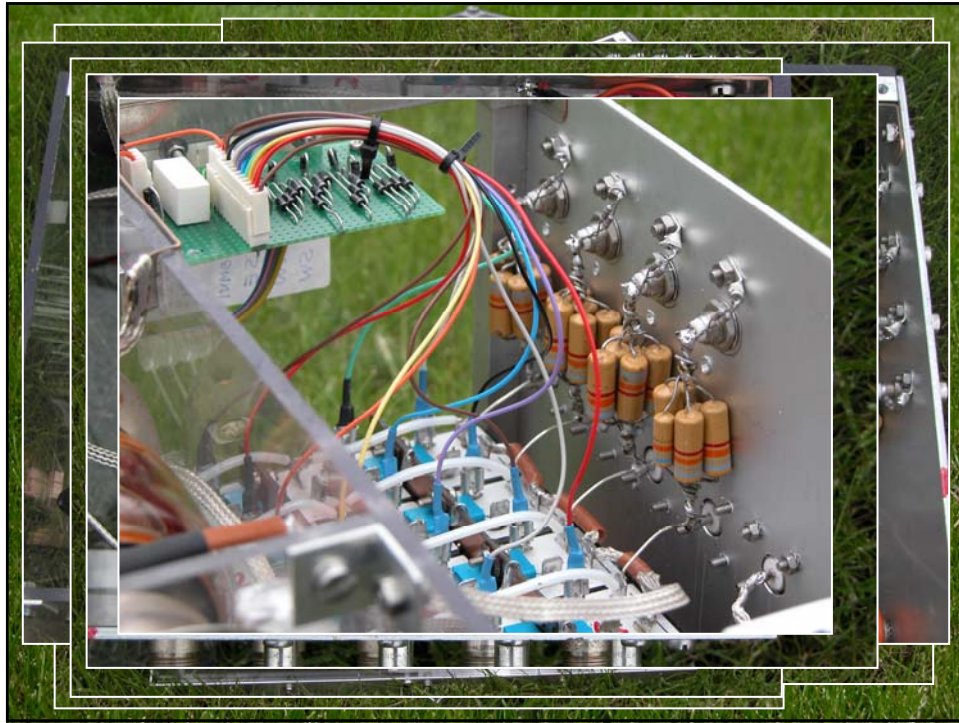

## INSTALLING AND TUNING



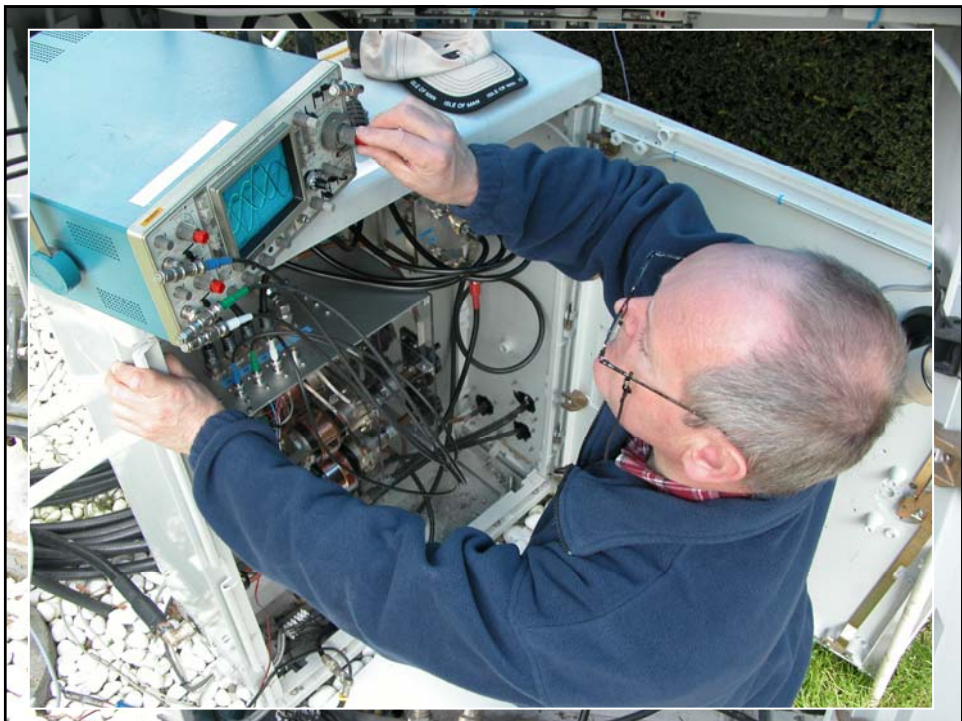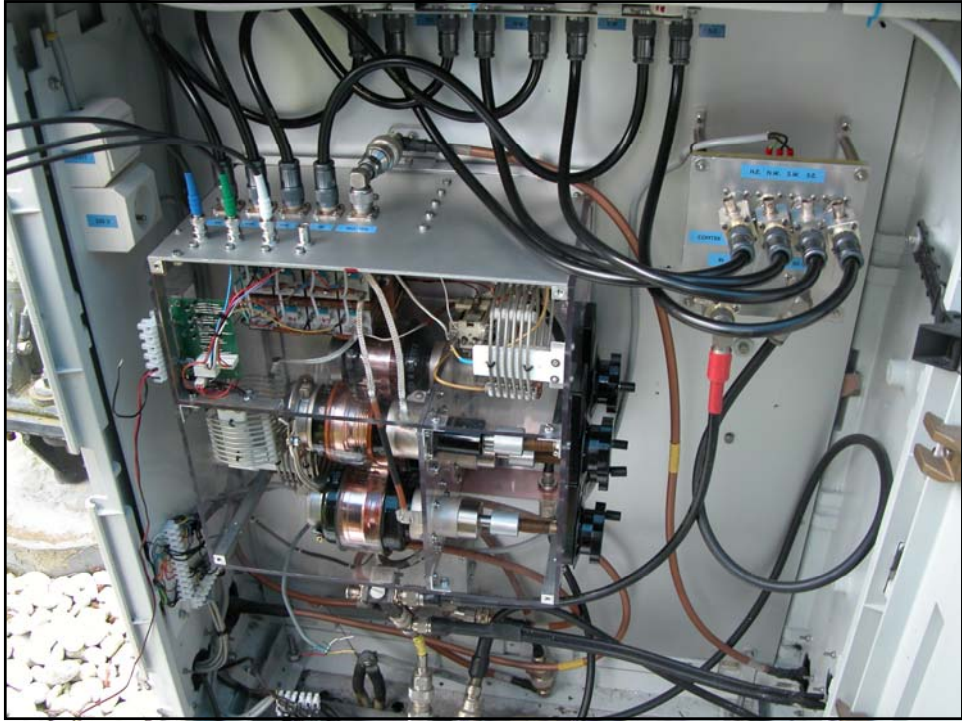

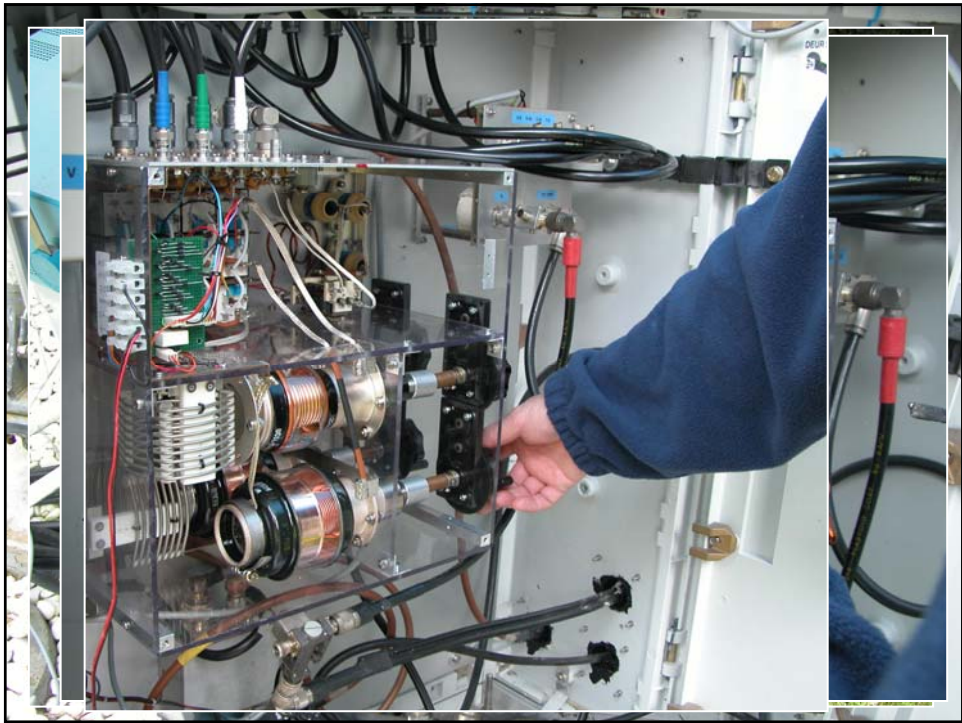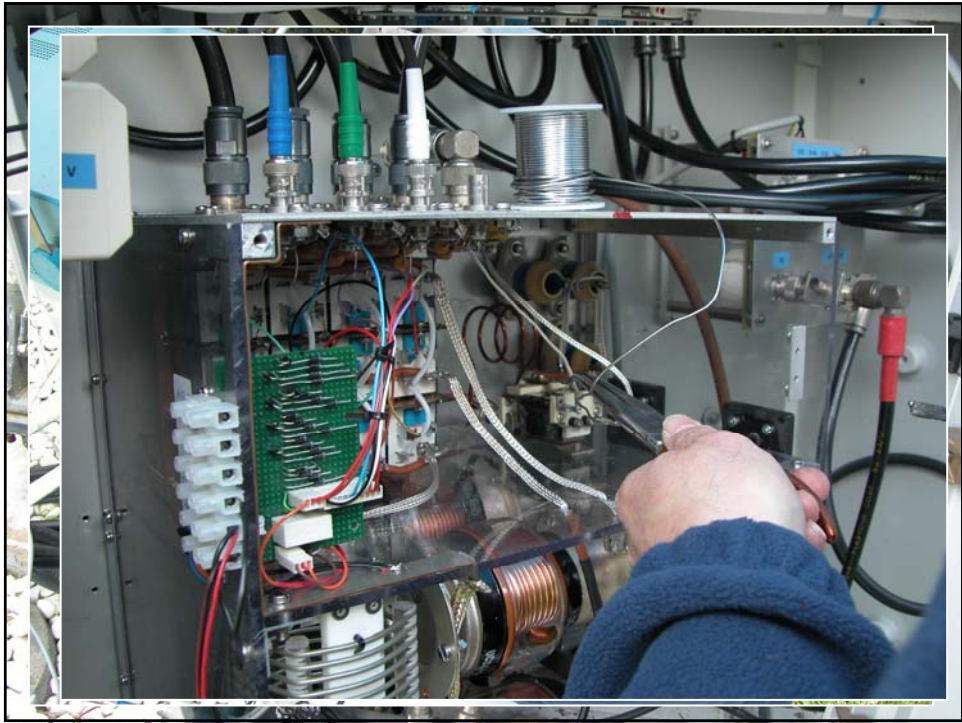

## MEASURED WITH NETWORK ANALYZER

TARGET	1.11	- 111 °	1.66	- 218 °
--------	------	---------	------	---------

ON 3.5 MHz

	K1	$\phi 1$	K2	$\phi 2$
NW	1.08	-116 °	1.69	- 226 °
SE	1.3	- 108 °	1.75	- 225 °
NE	1.2	- 103 °	1.72	- 223 °
SW	1.16	- 109 °	1.69	- 226 °

Accuracy: phase +/- 1°, amplitude +/- 1 %

Measurements done using an HP network analyzer

## IMPORTANT !

### IMPORTANT TO REMEMBER:


- YOU MUST MODEL YOUR ANTENNA AS PRECISELY AS POSSIBLE
- THIS WILL GIVE YOU APPROXIMATE L-NETWORK VALUES
- YOU NEED TO ADJUST THOSE IN THE FIELD
- **CONTINUOUSLY** ADJUSTABLE L AND C ELEMENTS ARE A MUST
- A 3 CHANNEL SCOPE IS A GOOD TOOL

# ALTERNATIVE ALIGNMENT PROCEDURE
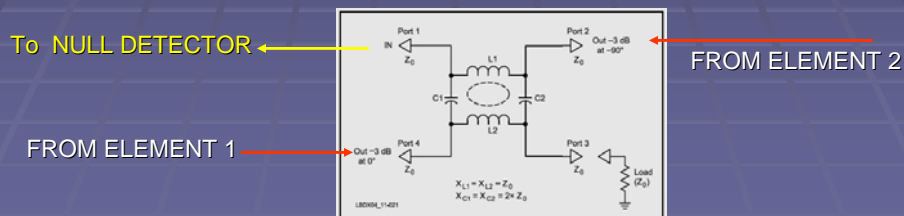
## W1MK HYBRID ALIGNMENT SETUP


This setup is used in conjunction with the W1MK detector / power meter

- A null method (bridge method)
- Using a hybrid coupler network




Already described in edition 3 of Low Band Dx-ing

# W7EL PHASE ADJUSTMENT (QUADRATURE)

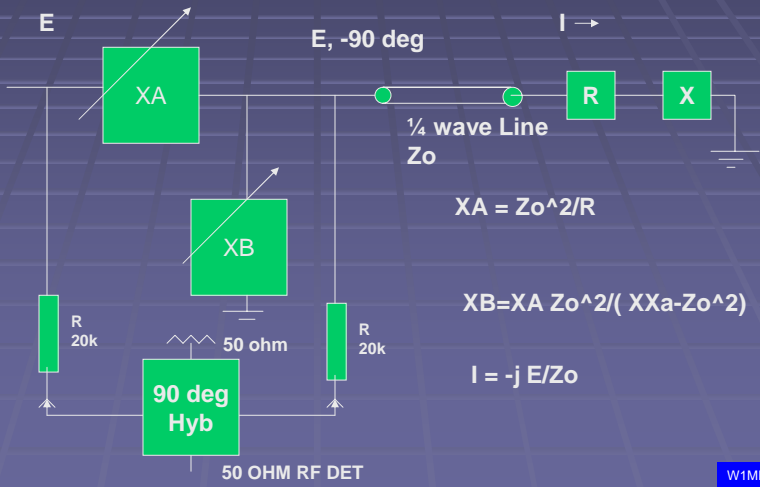

W1MK

# QUADRATURE HYBRID BRIDGE

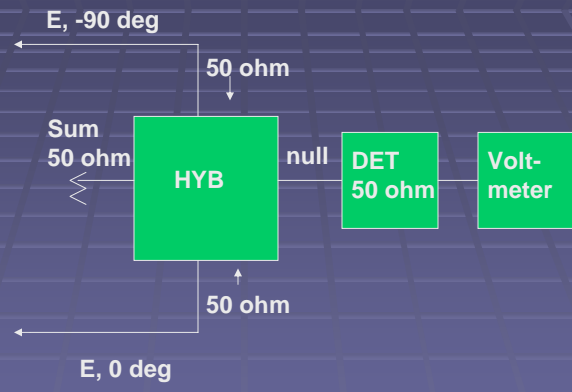

W1MK

# ERROR PLOT


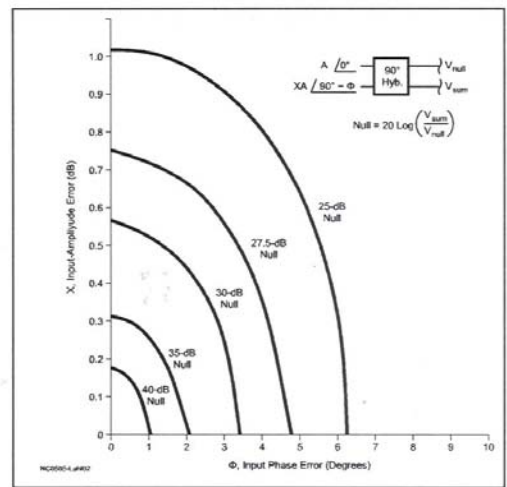


Figure 2—Amplitude and phase errors for various amounts of null.

W1MK


# NON QUADRATURE SETUP

WA3FET -111 DEG PHASE ANGLE

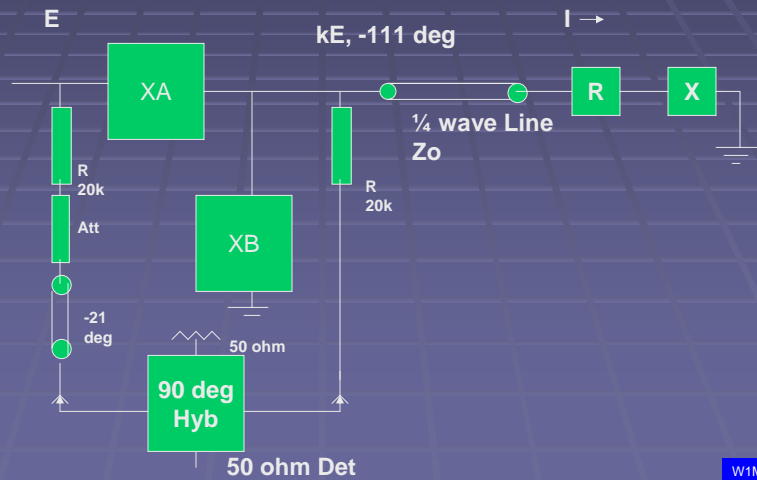


W1MK


# NON QUADRATURE SETUP

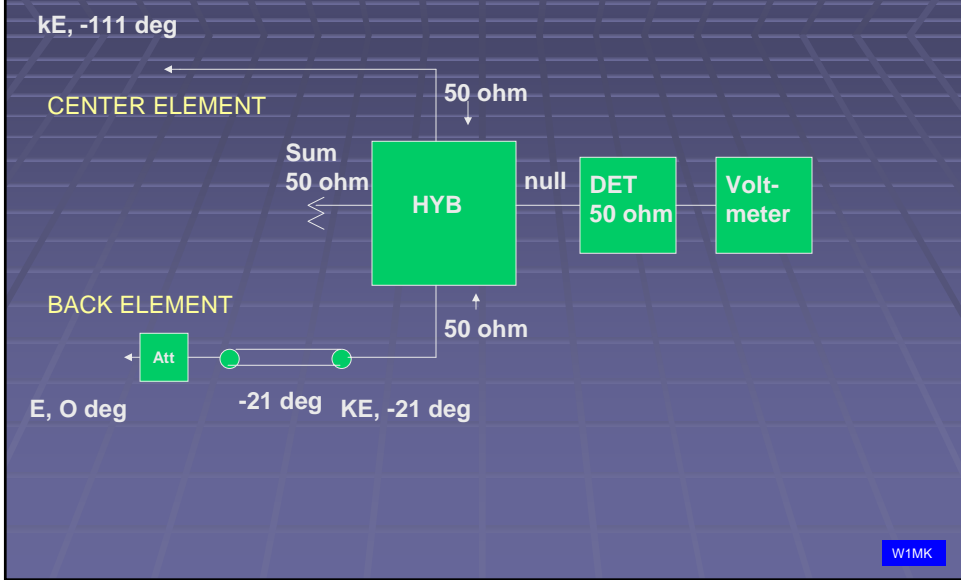

# NON QUADRATURE SETUP

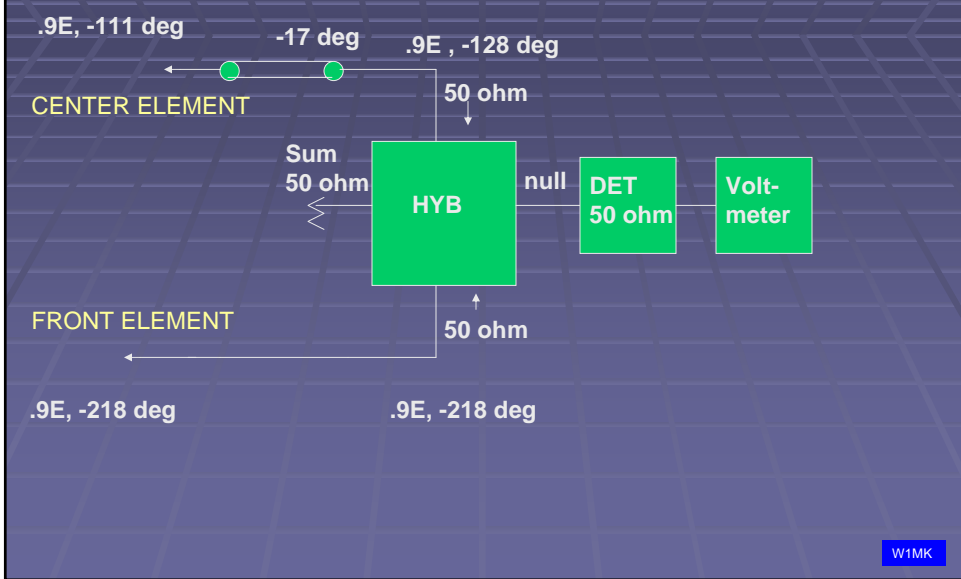

# W1MK DUAL POWER METER-DETECTOR

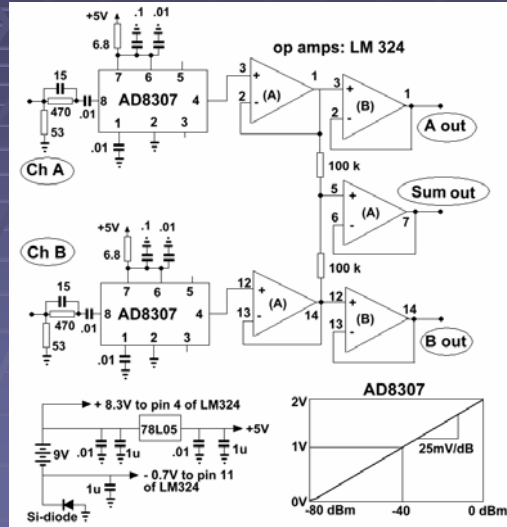


per W7ZOI

© ON4UN

W1MK

# W1MK DUAL POWER METER-DETECTOR

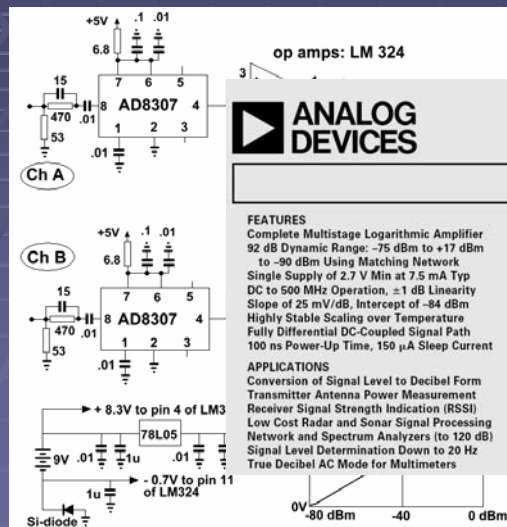

per W7ZOI

© ON4UN

W1MK




Low Cost DC-500 MHz, 92 dB Logarithmic Amplifier

AD8307


**FEATURES**  
 Complete Multistage Logarithmic Amplifier  
 92 dB Dynamic Range: -75 dBm to +17 dBm to -90 dBm Using Matching Network  
 Single Supply of 2.7 V Min at 7.5 mA Typ  
 DC to 500 MHz Operation,  $\pm 1$  dB Linearity  
 Slope of 25 mV/dB, Intercept of -84 dBm  
 Highly Stable Scaling over Temperature  
 Fully Differential DC-Coupled Signal Path  
 100 ns Power-Up Time, 150  $\mu$ A Sleep Current

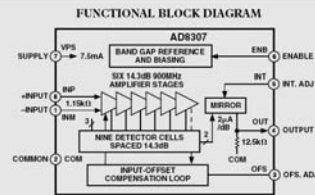**APPLICATIONS**  
 Conversion of Signal Level to Decibel Form  
 Transmitter Antenna Power Measurement  
 Receiver Signal Strength Indication (RSSI)  
 Low Cost Radar and Sonar Signal Processing  
 Network and Spectrum Analyzers (to 120 dB)  
 Signal Level Determination Down to 20 Hz  
 True Decibel AC Mode for Multimeters





# W1MK DUAL POWER METER-DETECTOR

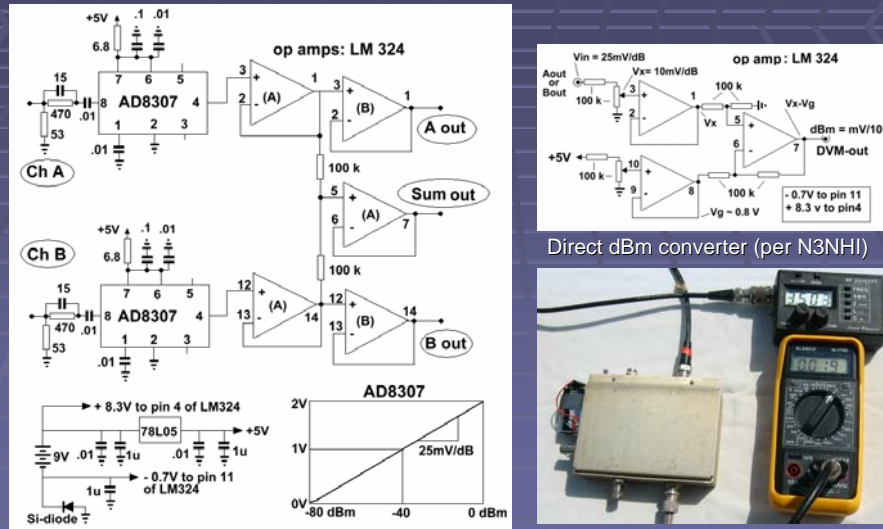

# W1MK ALIGNMENT SETUP

## ADVANTAGES

- SMALL DRIVING POWER REQUIRED (1 W)
- BATTERY POWER OPERATED
- INEXPENSIVE TEST/MEASURING EQUIPMENT
- NULL METHOD = INCREASED ACCURACY

## ***W1MK ALIGNMENT SETUP***

### **DRAWBACKS**

- VISUALLY “LESS INSTRUCTIVE”

### **CONCLUSION**

- SCOPE AND NULL-METHOD IN REALITY  
HAVE COMPARABLE ACCURACY

© ON4UN

W1MK

***BACK TO  
OUR ARRAY***

© ON4UN


## ***WHAT IS IMPORTANT***

- IDENTICAL ELEMENTS
  - AVOID COUPLING WITH OTHER ANTENNAS
  - ERECT THE ARRAY IN THE CLEAR
- QUARTER WAVE LINES MUST BE  $\lambda/4$  (AT BOTH BAND ENDS)
- BUILD THE ARRAY WITH GREAT CARE
- CAREFULLY ADJUST L NETWORK USING SCOPE OR W1MK HYBRID SETUP

© ON4UN
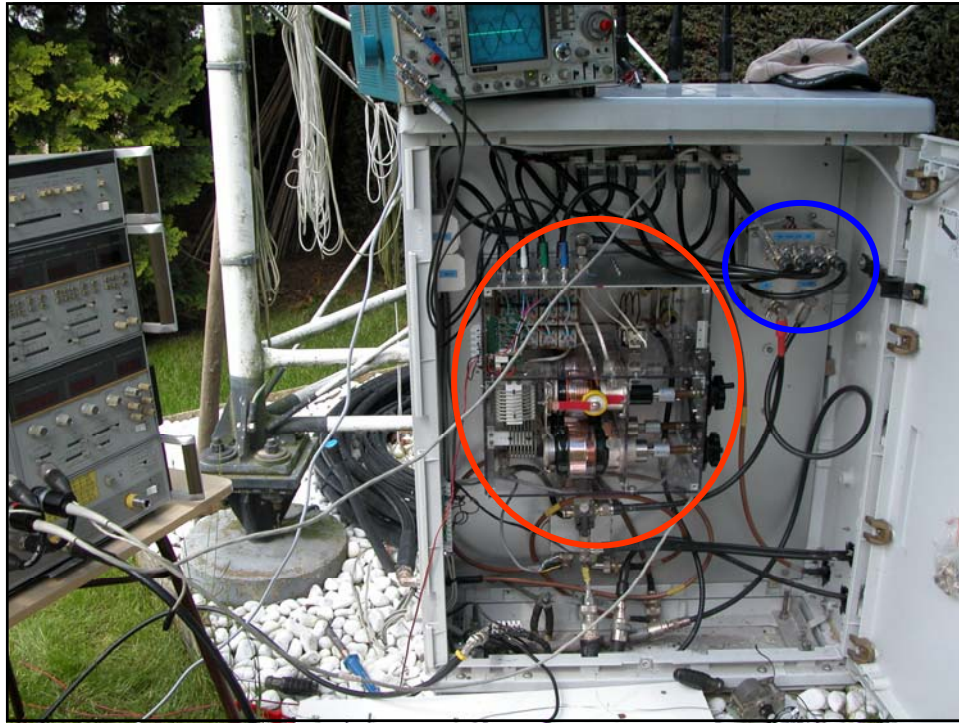
## ***COMPARING***

THE HYBRID (COMTEK)  
AND  
THE LAHLUM SYSTEM



## THE HYBRID COUPLER

<b>TARGET</b>	<b>1.0</b>	<b>-90°</b>	<b>1.0</b>	<b>-180°</b>
---------------	------------	-------------	------------	--------------

**ON 3.5 MHz**

	<b>K1</b>	<b>φ1</b>	<b>K2</b>	<b>φ2</b>
<b>NW</b>	1.02	-106 °	1.0	- 186 °
<b>SE</b>	1.01	- 96 °	1.03	- 188 °
<b>NE</b>	1.0	- 93 °	1.02	- 187 °
<b>SW</b>	1.0	- 100 °	1.0	- 186 °

Accuracy: phase +/- 1 degree, magnitude +/- 1 %

Measurements done using an HP network analyzer on a Comtek unit

## THE HYBRID COUPLER

TARGET	1.0	-90°	1.0	-180°
--------	-----	------	-----	-------

ON 3.8 MHz

	K1	$\phi 1$	K2	$\phi 2$
NW	1.2	- 92	1.02	- 192 °
SE	1.0	- 92	1.07	- 192 °
NE	1.24	- 86	1.07	- 193 °
SW	1.07	- 93	1.06	- 194 °

Accuracy: phase +/- 1 degree, magnitude +/- 1 %

Measurements done using an HP network analyzer on a Comtek unit

## THE HYBRID COUPLER

### OPERATIONAL BANDWIDTH

- OPERATIONAL BW: > 300 kHz (on 80m)
- SWR BW > 300 KHz
- POWER IN DUMMY LOAD: < 80 W on 3.5 MHz and < 25 W on 3.8 MHz (for 1.5 KW input)

... IF ELEMENTS AND QUARTER-WAVE FEED LINES ARE ALTERNATIVELY TUNED TO LOW END (CW) OR HIGH END (SSB) OF THE BAND

# ***THE HYBRID COUPLER***

**(Comtek unit)**

- “PLUG AND PLAY”
- BROADBAND (CW and Phone on 80m if quarter wave feed lines are “retuned”)
- RELIABLE
- NOT EXPENSIVE
  
- NO NEED FOR ALIGNMENT

**.... BUT QUADRATURE ONLY**

© ON4UN

# ***THE LAHLUM SYSTEM***

- POTENTIAL FOR 0.7 dB MORE GAIN AND IMPROVED DIRECTIVITY
- FAIRLY NARROW OPERATIONAL BANDWIDTH:  
CW AND PHONE ON 80: NEED TO “TUNE” THE QUARTER-WAVE FEED LINES AND ADJUST THE L-NETWORKS!
- REQUIRES ALIGNMENT IN THE FIELD

**... BUT FULL DESIGN FREEDOM (ANY ANGLE AND MAGNITUDE) and THE ONLY SOLUTION FOR MANY ARRAYS OTHER THAN 4-SQUARES**

© ON4UN

## ***NEW FEED SYSTEM FOR ARRAYS***

### ***WRAP UP***

- W1MK DEVELOPED THE MATHEMATICS GIVING FULL DESIGN FREEDOM (ANY MAGNITUDE/PHASE)
- THE LAHLUM FEED SYSTEM WAS APPLIED TO ON4UN'S 4-SQUARE
- SUITABLE ALIGNMENT METHODS WERE DEVELOPED AND DOCUMENTED
- A NEW FULLY FLEXIBLE FEED BOX WAS DESIGNED AND CONSTRUCTED
- TESTING WAS DONE ON BOTH QUADRATURE (HYBRID) AND LAHLUM (OPTIMIZED AMP/PHASE) CONFIGURATION
- CONCLUSIONS WERE DRAWN

© ON4UN

## ***NEW FEED SYSTEM FOR ARRAYS***

***THANK YOU,..  
ROGER, ON6WU  
AND  
ROBYE, W1MK***

© ON4UN

**NEW FEED SYSTEM FOR ARRAYS**

**THANK YOU**  
**FOR YOUR KEEN INTEREST**

© ON4UN

By John Devoldere, ON4UN  
Robye Lahlum, W1MK  
Roger Vermet, ON6WU